

Calculs de
iAPP



Calcul du filtre passe-bas:

$$S \rightarrow \frac{1}{w_c}$$

$$K := 1 = \frac{R_2}{R_1} \text{ donc } R_2 = R_1$$

Var table

$$\frac{V_{SO}}{V_{EN}} = H(s) = \frac{-K w_c^2}{s^2 + \frac{w_c}{Q}s + w_c^2}$$

$$w_c^2 = \frac{1}{R_2 R_3 C_2 C_3}$$

$$\frac{w_c}{Q} = 1,4141$$

$$w_c^2 = 700 \text{ Hz} \cdot 2\pi = 1400\pi \quad \rightarrow \quad \frac{-1 \cdot 1400\pi}{s^2 + 1,4141s + 1400\pi}$$

$$1,4141 = \frac{1}{100 \cdot 10^{-9}} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \quad \rightarrow R_1 = R_2$$

$$|H(s)| = \frac{1}{100 \cdot 10^{-9}} \left(\frac{2}{R_2} + \frac{1}{R_3} \right)$$

$$w_c^2 = \frac{1}{R_2 R_3 C_2 C_3} = 1400\pi$$

$$\frac{1}{R_2 R_3 \cdot 2,2 \cdot 10^{-5}} = 1400\pi$$

$$\frac{1}{R_2 R_3} = 3,08 \pi \cdot 10^{-12}$$

$$\frac{1}{3,08 \pi \cdot 10^{-12} R_3} = R_3$$

$$1.4141 = \frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$C_2 = 100 \text{ nF}$$

$$R_1 = R_2 = 4750 \Omega$$

$$R_3 = ?$$

$$C_3 = 22 \text{ nF}$$

$$1.4141 = \frac{1}{100 \cdot 10^{-9}} \left(\frac{1}{4750} + \frac{1}{4750} + \frac{1}{R_3} \right)$$

$$1400 \cdot 10^9 = \frac{1}{22 \cdot 10^{-9} \cdot 100 \cdot 10^{-9} \cdot 4750 \cdot R_3}$$

$$0.000000141 = 0.000421052 + \frac{1}{R_3}$$

$$0.00020244 R_3 = 1$$

$$-0.00042041 = \frac{1}{R_3}$$

$$R_3 = 4946,84$$

$$-2375,80 = R_3$$

$$\text{Passer Haut } 1000 \text{ Hz} : H(s) = \frac{s^2}{s^2 + 2828,2\pi s + (2000\pi)^2}$$

$$\text{Passer-bas } 5000 \text{ Hz} : H(s) = \frac{(10000\pi)^2}{s^2 + 444285 + (10000\pi)^2}$$

$$986 \ 960 \ 440 \ s^2$$

$$(s^2 + 2828,2\pi s + 39478417)(s^2 + 444285s + 986960440)$$

$$\begin{aligned} s^4 &+ 44428s^3 + 986960440s^2 \\ 8885s^3 &+ 394745105s^2 + 8,76 \cdot 10^{12}s \\ 39478417s^2 &+ 1,75 \cdot 10^{13}s + 3,90 \cdot 10^{16} \end{aligned}$$

$$\frac{986 \ 960 \ 440 \ s^2}{s^4 + 53313s^3 + 1421183962s^2 + 1,051 \cdot 10^{13}s + 3,90 \cdot 10^{16}} = H(s)$$

$$H_{BS} \text{ Bande} = \frac{986 \cdot 960 \cdot 440 \cdot \underline{\zeta^2}}{\underline{\zeta^4} + 53313 \cdot \underline{\zeta^3} + 1,421 \cdot 10^9 \cdot \underline{\zeta^2} + 1,05 \cdot 10^{13} \cdot \underline{\zeta} + 3,90 \cdot 10^{16}}$$


Au maximum on est à la fréquence 4650 Hz. Dans le passe bande à 4650 Hz on est à -2.08 dB donc nous on veut 1 dB donc +1 -1.08 dB

$$\frac{-1.08}{20} = A_V \quad A_V \approx 0.8830 \quad \text{Gain} = \frac{0.47}{0.88}$$

On connaît R_{71} donc 0.8830 53793

$$0.8830 = \frac{47500}{R_{25}} \quad 59375 \\ 59823$$
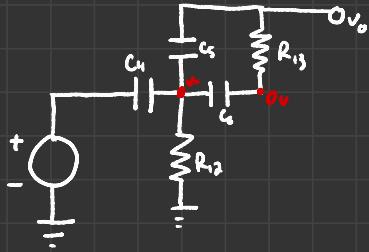
$$R_{25} = 53793.88 \Omega \quad 60352 \\ 55232$$



$$C_4 = C_5 = C_6 = 1 \text{ nF}$$

$$R_{13} = 34\,000 \Omega$$

$$R_{12} = 7500 \Omega$$

$$I_{C_6} = I_{R_{13}}$$

$$\frac{V_x}{V_s C} = -\frac{V_s}{R_{13}}$$

$$V_x = \frac{-V_s}{R_{13} C}$$

$$I_{C_4} = I_{R_1} + I_{C_5} + I_{R_{13}}$$

$$(V_e - V_x) C = \frac{V_x}{R_{12}} + (V_x - V_s) C - \frac{V_s}{R_{13}}$$

$$V_e C - V_x C = \frac{V_x}{R_{12}} + V_x C - V_s C - \frac{V_s}{R_{13}}$$

$$V_e C + \frac{V_s}{R_{13}} = \frac{V_x}{R_{12}} + V_x C + V_x C$$

$$= V_x \left(\frac{1}{R_{12}} + 2C \right) = \frac{-V_s}{R_{13} C} \left(\frac{1}{R_{12}} + 2C \right)$$

$$V_e C = \frac{-V_s}{R_{13} R_{12} C} - \frac{2V_s}{R_{13}} - \frac{V_s}{R_{13}} - V_s C$$

$$V_C SC = \frac{-Vs}{R_{13} R_{12} SC} + \frac{3Vs}{R_{13}} - Vs SC$$

$$V_C SC = Vs \left(\frac{-1}{R_3 R_2 SC} - \frac{3}{R_{13}} - SC \right)$$

$$V_C = Vs \left(\frac{-1}{R_3 R_2 (SC)^2} - \frac{3}{R_3 SC} - 1 \right)$$

$$\frac{\frac{1}{-1} - \frac{3}{R_3 SC} - 1}{\frac{1}{R_3 R_2 (SC)^2} - \frac{3}{R_3 SC} - 1} = \frac{Vs}{V_C} \cdot -s^2$$

$$\frac{-s^2}{s^2 + \frac{3}{R_3 C} s + \frac{1}{R_3 R_2 C^2}} = H(s)$$

$$\frac{-\zeta^2}{s^2 + \frac{3}{R_3 C} s + \frac{1}{R_3 R_2 C^2}} = H_{4s}$$

$$\zeta = 2000 \pi j$$

$$H_{4s} = -3 \text{ dB} = 0.707$$

$$R_{13} = 340 \ 000 \Omega$$

$$X = \frac{(2000\pi)^2}{-(2000\pi)^2 + 17647058\pi J + \frac{2.94 \cdot 10^{12}}{R_{12}}}$$

$$- X w^2 + \frac{3x}{R_3 C} w + \frac{X}{R_3 R_2 C^2} = w^2$$

$$R_{12} = \frac{1}{(w^2 + Xw^2) - \frac{3x}{R_3 C} w + \frac{R_3 C^2}{X}}$$

Sinus

Calcul Sommateur:

$$H_{(1)}_{\text{Bende}} = \frac{986 \cdot 960 \cdot 440 \cdot s^2}{s^4 + 53 \cdot 313 \cdot s^3 + 1431 \cdot 183 \cdot 960 \cdot s^2 + 1.051 \cdot 10^{13} \cdot s + 3.90 \cdot 10^{16}} = \frac{A}{B + C + D + E + F}$$

$$H_{(1)}_{\text{bos}} = \frac{(1400 \cdot n)^2}{s^2 + 6219 \cdot s + (1400 \cdot n)^2} = \frac{G}{H + I + J}$$

$$H_{(1)}_{\text{heat}} = \frac{s^2}{s^2 + 19747 \cdot 15 + (1400 \cdot n)^2} = \frac{K}{L + M + N}$$

En parallèle c'est une addition Δ

Numerateur:

$$A(H+I+J)(L+M+N) + G(B+L+D+E+F)(L+M+N) + K(H+I+J)(B+C+D+E+F)$$

$$= AHL + AHM + AHN + AIL + AIM + AIN + AJL + AJM + AJN + GBL + GBM + GBN + GCL + GCM + GDN \\ + GDL + GDM + GDN + GEL + GEM + GEN + GFL + GFM + GFN + KBH + KBI + KBJ + KCH + KCI + KCJ \\ + KOH + KDI + KDJ + KEH + KET + KEJ + KFH + KFI + KFJ$$

$$986 \cdot 960 \cdot 440 \cdot s^6 + 6.13 \cdot 10^{13} \cdot s^5 + 1.90 \cdot 10^{18} \cdot s^4$$

$$+ 6.13 \cdot 10^{12} \cdot s^5 + 3.8 \cdot 10^{17} \cdot s^4 + 1.9 \cdot 10^{23} \cdot s^3$$

$$1.9 \cdot 10^7 \cdot s^6 + 1.20 \cdot 10^{12} \cdot s^5 + 3.7 \cdot 10^{16} \cdot s^4 \\ + 1.9 \cdot 10^{16} \cdot s^4 + 1.9 \cdot 10^{21} \cdot s^3 + 3.7 \cdot 10^{25} \cdot s^2$$

$$158 + 6219 \cdot s^7 + 53313 \cdot s^7 \\ + 1.03 \cdot 10^{13} \cdot s^5 + 6.4 \cdot 10^{16} \cdot s^4 + 1.99 \cdot 10^{19} \cdot s^3 \\ + 2.7 \cdot 10^{16} \cdot s^4 + 2.7 \cdot 10^{21} \cdot s^3 + 5.3 \cdot 10^{25} \cdot s^2 \\ + 2.0 \cdot 10^{20} \cdot s^3 + 1.3 \cdot 10^{25} \cdot s^2 + 3.9 \cdot 10^{29} \cdot s^1 \\ + 7.5 \cdot 10^{23} \cdot s^2 + 4.7 \cdot 10^{26} \cdot s^1 + 1.45 \cdot 10^{33}$$

$$1.9 \cdot 10^7 \cdot s^6$$

$$3.3 \cdot 10^8 \cdot s^6 + 1.03 \cdot 10^{10} \cdot s^5$$

$$1.4 \cdot 10^9 \cdot s^6 + 8.8 \cdot 10^{12} \cdot s^5 + 2.7 \cdot 10^{16} \cdot s^4 \\ + 1.0 \cdot 10^{13} \cdot s^5 + 6.5 \cdot 10^{16} \cdot s^4 + 2.0 \cdot 10^{20} \cdot s^3 \\ + 3.9 \cdot 10^{16} \cdot s^4 + 2.4 \cdot 10^{20} \cdot s^3 + 7.5 \cdot 10^{23} \cdot s^2$$

$$s^8 + 5.9 \cdot 10^4 \cdot s^7 + 2.7 \cdot 10^9 \cdot s^6 + 8.95 \cdot 10^3 \cdot s^5 + 2.5 \cdot 10^{18} \cdot s^4 + 2.26 \cdot 10^{23} \cdot s^3 + 1.75 \cdot 10^x \cdot s^2 \\ + 4.37 \cdot 10^{24} \cdot s + 1.45 \cdot 10^{33}$$